

# **ENT-AN0114 Application Note**

## **SimpliPHY Transformerless Ethernet Designs**



**Microsemi Corporate Headquarters**

One Enterprise, Aliso Viejo,  
CA 92656 USA

Within the USA: +1 (800) 713-4113

Outside the USA: +1 (949) 380-6100

Sales: +1 (949) 380-6136

Fax: +1 (949) 215-4996

E-mail: [sales.support@microsemi.com](mailto:sales.support@microsemi.com)

[www.microsemi.com](http://www.microsemi.com)

© 2006–2016 Microsemi Corporation.  
All rights reserved. Microsemi and the  
Microsemi logo are trademarks of  
Microsemi Corporation. All other  
trademarks and service marks are the  
property of their respective owners.

Microsemi makes no warranty, representation, or guarantee regarding the information contained herein or the suitability of its products and services for any particular purpose, nor does Microsemi assume any liability whatsoever arising out of the application or use of any product or circuit. The products sold hereunder and any other products sold by Microsemi have been subject to limited testing and should not be used in conjunction with mission-critical equipment or applications. Any performance specifications are believed to be reliable but are not verified, and Buyer must conduct and complete all performance and other testing of the products, alone and together with, or installed in, any end-products. Buyer shall not rely on any data and performance specifications or parameters provided by Microsemi. It is the Buyer's responsibility to independently determine suitability of any products and to test and verify the same. The information provided by Microsemi hereunder is provided "as is, where is" and with all faults, and the entire risk associated with such information is entirely with the Buyer. Microsemi does not grant, explicitly or implicitly, to any party any patent rights, licenses, or any other IP rights, whether with regard to such information itself or anything described by such information. Information provided in this document is proprietary to Microsemi, and Microsemi reserves the right to make any changes to the information in this document or to any products and services at any time without notice.

**About Microsemi**

Microsemi Corporation (Nasdaq: MSCC) offers a comprehensive portfolio of semiconductor and system solutions for aerospace & defense, communications, data center and industrial markets. Products include high-performance and radiation-hardened analog mixed-signal integrated circuits, FPGAs, SoCs and ASICs; power management products; timing and synchronization devices and precise time solutions, setting the world's standard for time; voice processing devices; RF solutions; discrete components; enterprise storage and communication solutions, security technologies and scalable anti-tamper products; Ethernet solutions; Power-over-Ethernet ICs and midspans; as well as custom design capabilities and services. Microsemi is headquartered in Aliso Viejo, Calif., and has approximately 4,800 employees globally. Learn more at [www.microsemi.com](http://www.microsemi.com).

# Contents

---

<b>1</b>	<b>Revision History</b>	<b>1</b>
1.1	Revision 1.2	1
1.2	Revision 1.1	1
1.3	Revision 1.0	1
<b>2</b>	<b>Overview</b>	<b>2</b>
2.1	Typical Ethernet Application using Transformers	2
2.2	Transformerless Applications	2
<b>3</b>	<b>Transformerless Design</b>	<b>3</b>
3.1	Connecting Two SimpliPHYs Together	3
3.2	Connecting a SimpliPHY to an External Common-Mode PHY	3

# Figures

---

Figure 1	Typical Ethernet Application Using a Transformer .....	2
Figure 2	Transformerless Ethernet Application .....	2
Figure 3	Connecting Two SimpliPHYs Together .....	3
Figure 4	Connecting a SimpliPHY to an Externally Biased Line Driver (Acceptable Method) .....	4
Figure 5	Connecting a SimpliPHY to an Externally Biased Line Driver (Preferred Method) .....	4

# 1 Revision History

---

The revision history describes the changes that were implemented in the document. The changes are listed by revision, starting with the most current publication.

## 1.1 Revision 1.2

The following is a summary of the changes in revision 1.2 of this document.

- Diagrams of third-party PHY termination were corrected. For more information, see [Figure 4](#), page 4 and [Figure 5](#), page 4.
- Details about backplane applications were updated. For more information, see [Transformerless Applications](#), page 2.

## 1.2 Revision 1.1

In revision 1.1 of this document, the “Connecting a SimpliPHY to an Externally Biased Line Driver (Preferred Method)” diagram was updated. For more information, see [Figure 5](#), page 4.

## 1.3 Revision 1.0

Revision 1.0 was the first publication of this document.

## 2 Overview

This application note describes a specific application called Transformerless Ethernet. Transformerless Ethernet is used, primarily, for two purposes:

- To support backplane applications (such as PICMG)
- To support point-to-point on-board copper media Ethernet connections


Because of the line driver integral to Microsemi's SimpliPHY™ technology, Microsemi copper PHYs are ideal for use in Transformerless applications.

### 2.1 Typical Ethernet Application using Transformers

In a typical Ethernet application, connections between PHYs are made over unshielded twisted pair (UTP), 100  $\Omega$ , category 5E cable. The front-end interface components consist of a transformer, an RJ-45 connector, as well as several termination resistors and bypass capacitors.

The purpose of the transformer is to eliminate the incoming DC signal component introduced in the transmission signals as a result of different ground references between the two communicating entities. The transformer is not required if the communicating devices share a common ground and the transceivers do not use the magnetics for any other purpose (such as sourcing current or providing a common-mode voltage into the transceiver), which is typical of current-mode line driver PHYs.


**Figure 1 • Typical Ethernet Application Using a Transformer**

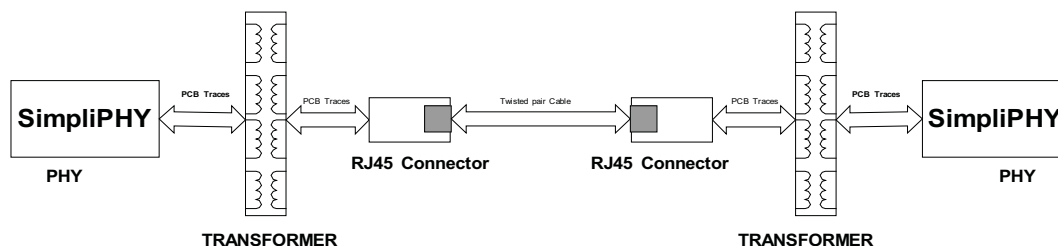

### 2.2 Transformerless Applications

When two copper PHYs are interconnected through printed circuit board traces (as opposed to UTP cable), there is no longer any need for a transformer. This interconnection can be either two PHYs on the same board (permanently linked together through signal traces), or it can be PHYs on blade cards connected together via backplane bus within a single chassis system. The removal of the transformer and the RJ45 connector allows for Bill of Material (BOM) cost savings and can simplify the PCB layout.

**Figure 2 • Transformerless Ethernet Application**

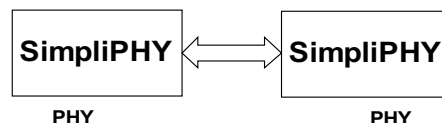

It is important to note that specifications developed by the PCI Industrial Computers Manufacturers Group (PICMG group) use Gigabit Ethernet transceivers on backplanes. As an example application, the AdvancedTCA® Base Interface specified in PICMG 3.0 could use a transformerless interface to implement board-to-board 10/100/1000 Mbps connectivity. For more information about the PICMG specification, see <http://www.picmg.org>.

## 3 Transformerless Design

Output line drivers of transceivers can be classified as current-mode or voltage-mode-based. Typical current-mode PHYs generate their output waveforms by sinking a current through the center tap of the primary winding of the transformer. The transformer is also used to provide the necessary common-mode voltage for the PHY.

On the other hand, SimpliPHY transceivers use voltage-mode drivers where a center tap voltage and current is not needed from the transformer. Therefore, SimpliPHY transceivers support transformerless 10/100/1000BASE-T operation without the addition of extra circuitry.


For more information about the differences between voltage-mode and common-mode-based PHYs, please refer to the SimpliPHY Advantages white paper.

It is important to differentiate the two line driver methods used by PHYs because the methods of connecting them together require slightly different design techniques, as described in the following sections.

### 3.1 Connecting Two SimpliPHYs Together

If two SimpliPHYs are on the same board design and they share the same ground reference, then the copper interfaces of the two PHYs can be directly connected together with 100  $\Omega$  differential PCB signal traces. If the PHYs are on different boards connecting over a backplane, consider adding series capacitors to prevent any common-mode mismatches.

**Figure 3 • Connecting Two SimpliPHYs Together**

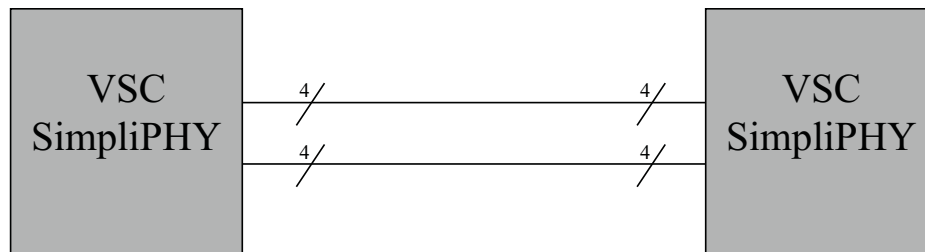

Connected with PCB Traces with the same ground reference


**Note:** If the PHYs are on different boards, add series capacitors.

### 3.2 Connecting a SimpliPHY to an External Common-Mode PHY

Unlike a SimpliPHY device, a current-mode PHY is an example of a PHY requiring a common-mode voltage. These PHYs have a distinct disadvantage with transformerless applications because of this legacy architecture.


The following illustrations show two methods that can be employed to work around this issue: an acceptable method and the preferred method.

**Figure 4 • Connecting a SimpliPHY to an Externally Biased Line Driver (Acceptable Method)**

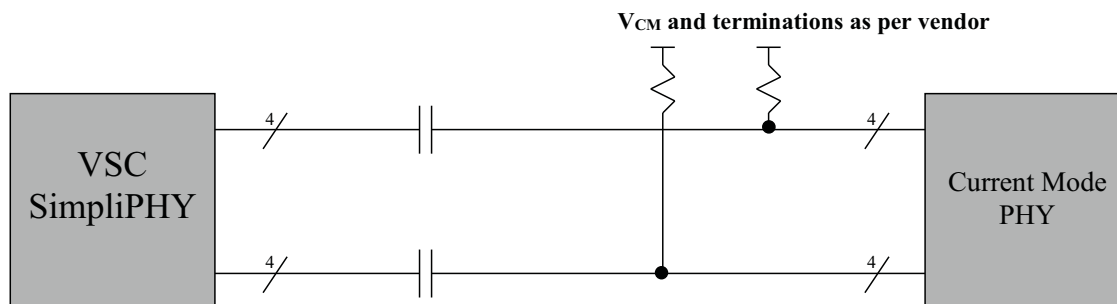

**WARNING:** A suitable common-mode termination strategy, as reflected in [Figure 4](#), page 4, must be verified by the non-Microsemi PHY vendor.

**Figure 5 • Connecting a SimpliPHY to an Externally Biased Line Driver (Preferred Method)**

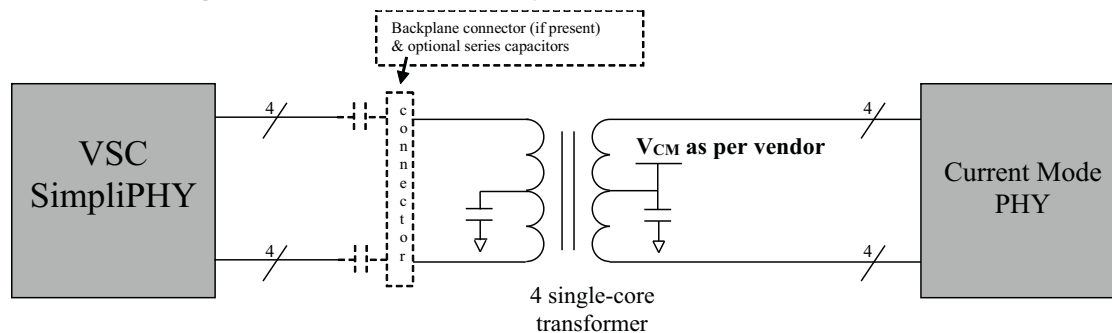

Both solutions address the need of the current-mode PHY requiring a common-mode voltage on its differential interface. The acceptable method may use pull-up resistors to emulate the use of the center tap of the transformer. Depending on the circuit topology inside the other PHY's line driver, additional circuit connections may be required.

The preferred method still employs a transformer. Because EMI and other issues usually corrected by a transformer connected to a cable are not present, a very simple 4-core (single core on 4-pairs) transformer can be used (as opposed to a standard 8 or 12-core magnetic).

If the two PHYs are on different boards (for instance, in a backplane application), then DC-blocking series capacitors are needed between the SimpliPHY device and the backplane connector. The 4-core transformer should be located on the card with the current-mode PHY.